

# Digital System Design using VHDL

## Final Exam-Group 3

Computer Engineering department, Iran University of Science and Technology


Time: 100 Minutes, Winter 2022

**Q1.** Using VHDL design a FSM that receives an n bit sequence serially and determine whether the sequence is symmetric or not. A symmetric sequence is a sequence that has the same from either is read from LSB to MSB or from MSB to LSB


11100111 is a symmetric sequence

10100111 is not symmetric

 **Q2.** Actel FPGAs are based on MUX-based units such as ACT1 module. Implement the following circuit with minimum number of Act1 module. What does the circuit do?




 **Q3.** Implement the following circuit with minimum number of LUT-3s



**Q4.** Given the following system, The LUT-6 implements the following function:  $OLUT = \lceil \sqrt{ILUT} \rceil$

A) complete the Timing Diagram.

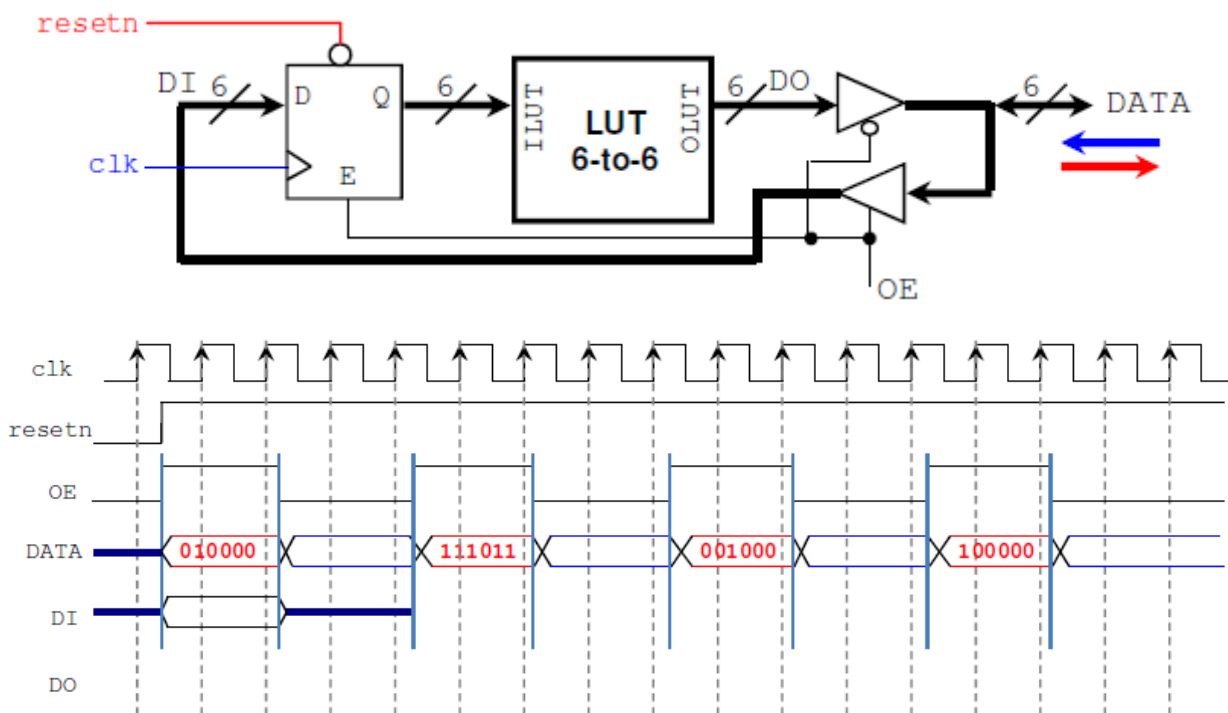

B) Re-implement the circuit using LUT-3s