

Digital System Design using VHDL


Final Exam-Group 4

Computer Engineering department, Iran University of Science and Technology


Time: 100 Minutes, Winter 2022

Q1. Using VHDL design a FSM that receive two separate sequence of bits (A and B) serially. The FSM machine each clock cycle randomly read from one of the sequences (perhaps two times read from sequence A). The output Z becomes one when you detect 01 in sequence A and then 10 in sequence B.

 
Q2. Implement the following circuit using LUT-3s.



 Q3. Consider the function of following PLA



 Convert it to the following PAL device. You can add another output to the following PAL device



Q4. Implement the following circuit using minimum number of Cool-Runner II macrocell.

